


# EECS 151/251A Homework 8

Due Friday, November 18<sup>th</sup>, 2022 11:59PM

## Problem 1: Carry Lookahead

Recall from the lecture that Kogge–Stone adder is a parallel prefix form carry look-ahead adder (CLA). In this problem, we'd like to design and analyze a 16-bit radix-4 Kogge–Stone adder.

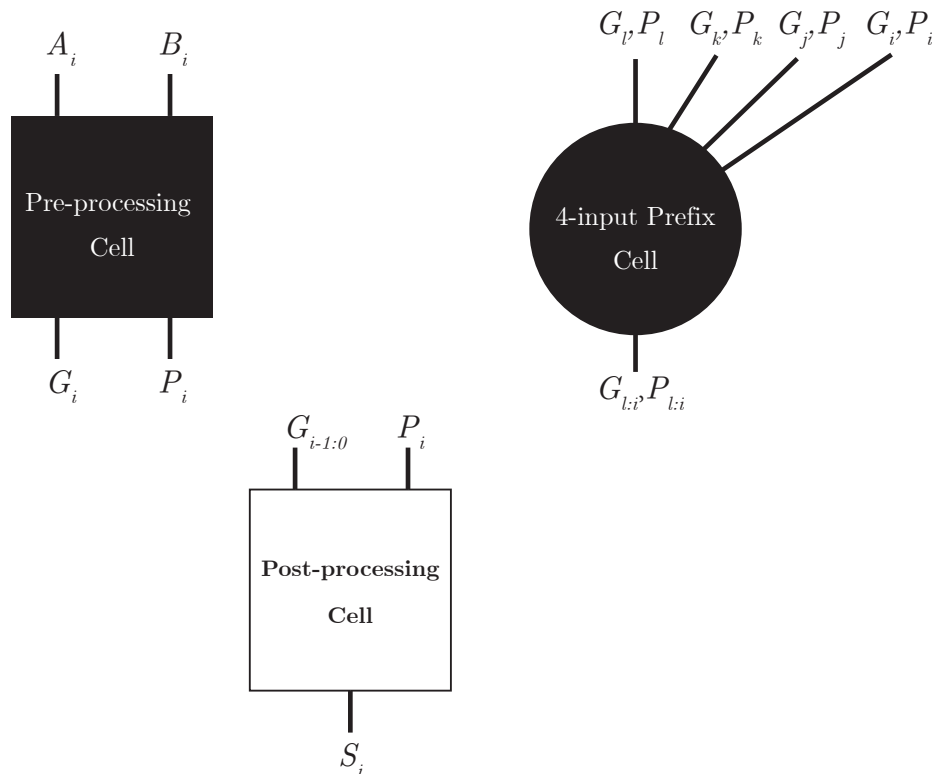- (a) Write down the Boolean functions of the gate implementation of following building blocks for the radix-4 Kogge–Stone adder. You may use *AND*, *OR* and *XOR* only. Also, how should you handle cases where certain 4-input prefix cells have fewer than 4 pairs of input?



**Solution:**

Pre-processing:  $G_i = A_i B_i, \quad P_i = A_i \oplus B_i$

4-input prefix:  $G_{l:i} = G_l + (P_l(G_k + (P_k(G_j + P_j G_i))))$   
 $P_{l:i} = P_l P_k P_j P_i$

Post-processing:  $S_i = P_i \oplus G_{i-1:0}$

If a prefix cell has only two or three pairs of input, then these input should be viewed as grounded (zero).

(b) Which of the following are true for radix-4 Kogge-Stone adder?

\_\_\_\_ Compared to Radix-2 adders, Radix-4 adders reduce the depth of the tree by a factor of 4 (excluding the input and output stages).

\_\_\_\_ An N-bit Radix-4 adders has  $\mathcal{O}(\sim \log_4(N))$  in time.

\_\_\_\_ It is possible to implement a 32-bit Kogge-Stone adder using only the building blocks in part (a).

**Solution:**

F. Radix-4 adders reduce the depth by a factor of 2.

T. But do keep in mind that each stage takes longer time.

T. You might need to leave some intermediate P,G outputs unconnected, though.

(c) Suppose given the following propagation delays:

$$t_{AND} = 5ps, \quad t_{OR} = 4ps, \quad t_{XOR} = 7ps$$

Derive the critical path of the 16-bit Kogge-Stone adder based on your implementation in part (a), ignoring the delays in routing. (Hint: If you are not sure about the topology, take a look at the slides in Lecture 19.)

**Solution:**

The longest path will go through: 1 pre-processing cell + 2 four-input prefix cells + 1 post-processing cell. So the total delay is:

$$\begin{aligned} t_{critical} &= \max\{5ps, 7ps\} + 2 \times (5ps + 4ps + 5ps + 4ps + 5ps + 4ps) + 7ps \\ &= 7ps + 2 \times 27ps + 7ps \\ &= 68ps \end{aligned}$$


(d) Based on your result above, what's the maximum clock frequency for this 16-bit adder?

**Solution:**

$$\begin{aligned} f_{max} &= 1/t_{critical} \\ &\approx 1.47 \times 10^{10} \text{ Hz} \\ &= 14.7 \text{ GHz} \end{aligned}$$

(e) **(251A Only)** In reality, those prefix cells will not be built using the basic 2-input AND, OR, XOR gates. Instead, they will be built as a big CMOS gate (and inverters). Draw the schematic of the 4-input prefix cell for  $\bar{G}_{l:i}$  and  $\bar{P}_{l:i}$  respectively with the minimum number of transistors.

Solution:

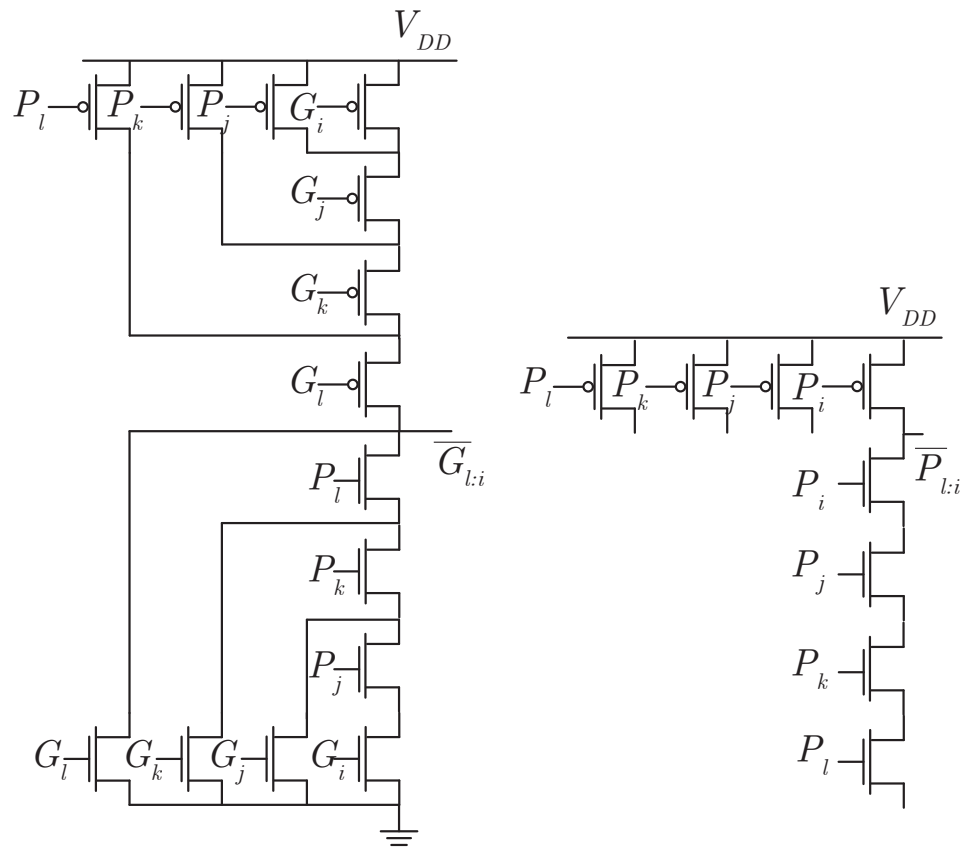

## Problem 2: Booth's Bizarre Invention

Refer to the following table of the behavior of Booth recoding.

$B_{K+1}$	$B_K$	$B_{K-1}$	Action
0	0	0	add 0
0	0	1	add A
0	1	0	add A
0	1	1	add 2A
1	0	0	sub 2A
1	0	1	sub A
1	1	0	sub A
1	1	1	add 0

Write down the sequence of operation and the final result given the following unsigned two input numbers:

$$\begin{array}{r} 01100111 \text{ (A)} \\ \times 10110010 \text{ (B)} \end{array}$$

Answer should be in the format of:

$$\begin{array}{ll} \text{Suppose } A=1010 & B=1001 \\ (B[1:-1]=010): & \text{add A,} \\ (B[3: 1]=100): & \text{sub 2A,} \\ & \dots \\ \text{result} & = A - (A \ll 2) + \dots \\ & = 0000(1010) - 00(1010)00 + \dots \\ & = \dots \end{array}$$

**Solution:**

$$\begin{array}{ll} (B[1:-1]=100): & \text{sub 2A,} \\ (B[3: 1]=001): & \text{add A,} \\ (B[5: 3]=110): & \text{sub A,} \\ (B[7: 5]=101): & \text{sub A,} \\ (B[9: 7]=001): & \text{add A} \\ \text{result} & = -(2A) + (A \ll 2) - (2A \ll 4) - (A \ll 6) + (A \ll 8) \\ & = - 0000000(01100111)0 + 000000(01100111)00 \\ & \quad - 0000(01100111)0000 - 00(01100111)000000 \\ & \quad + (01100111)00000000 \\ & = 0100 \ 0111 \ 1001 \ 1110 \text{ (18334 in decimal)} \end{array}$$