 


## EECS 151/251A Homework 6

Due Friday, November 4<sup>th</sup>, 2022 11:59PM

### Problem 1: CMOS Gates

- (a) What is the boolean expression for the function described by the CMOS gate below?




- (b) Draw the static complementary CMOS circuit that implements the following logic function:

$$\overline{ABC + DE}$$
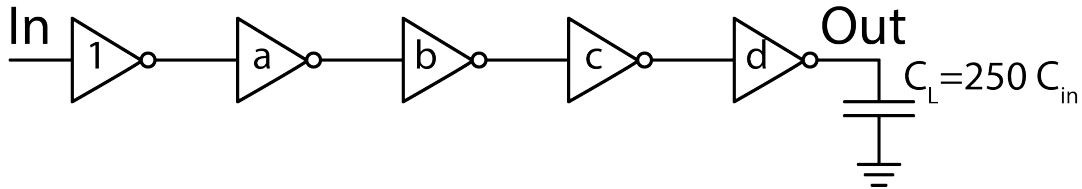
## Problem 2: Inverter Delay

We want to design a 5-stage inverter chain that can drive a load capacitance of  $C_L = 250C_{in}$  with the smallest delay possible, where  $C_{in}$  is the input capacitance of a minimum sized inverter. The first inverter is constrained to be minimum size ( $W = 1$  as in shown in the figure). Assume that  $\tau_{inv} = 10$  ps and  $\gamma = 1$ .



(a) How should the inverter chain be sized for minimum delay?

(b) What is the total delay through the inverter chain?

- (c) Assume that the number of stages is not restricted to 5. How many stages should you use for minimum delay? What is the total delay?

### Problem 3: Logical Effort

In the lecture, we mentioned that inverters in today's FinFET technology nodes have equal NMOS and PMOS widths since the  $R_{on,n} = R_{on,p}$ . Here, we assume a different technology, where for a minimum size transistor ( $W = 1$ ),


- NMOS on resistance  $R_{on,n} = R$
- PMOS on resistance  $R_{on,p} = 3R$
- Gate capacitance  $C_g = C$  (same for both NMOS and PMOS)

Assume  $\gamma = 1$ .

- (a) How should the minimum inverter be sized? Specify the NMOS width  $W_n$  and PMOS width  $W_p$ .

- (b) What is  $R_{eq}$  and  $C_{in}$  of the minimum size inverter?

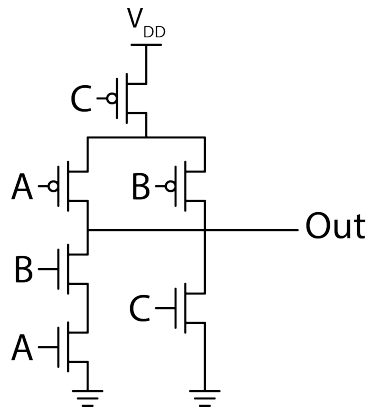(c) We want to design the following custom CMOS gate:



How should the custom gate be sized to have the same output current as the minimum size inverter?

(d) Compute the logical effort  $LE$  and (normalized) parasitic delay  $P$  of the custom gate.

*Note:* The logical effort should be calculated separately for each input.


$$LE_A =$$

$$LE_B =$$

$$LE_C =$$

$$P =$$

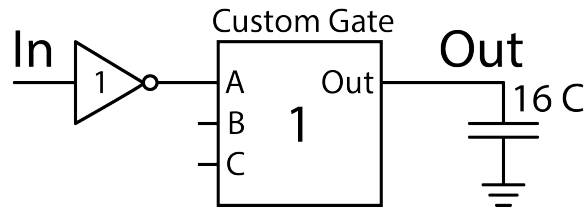(e) (251A Only) Suppose that we have the following data path:



An inverter drives the custom gate's input A, and the custom gate drives a load capacitance  $C_L = 16C$ . Both the inverter and custom gate are minimum size (as denoted by "1" in the figure). Assume that the custom gate's other inputs B and C are driven by other circuits not shown here.

What is the total delay from the input to the output? Express in terms of  $R$  and  $C$ .